

A Multistage Differential BJT Amplifier Simulation

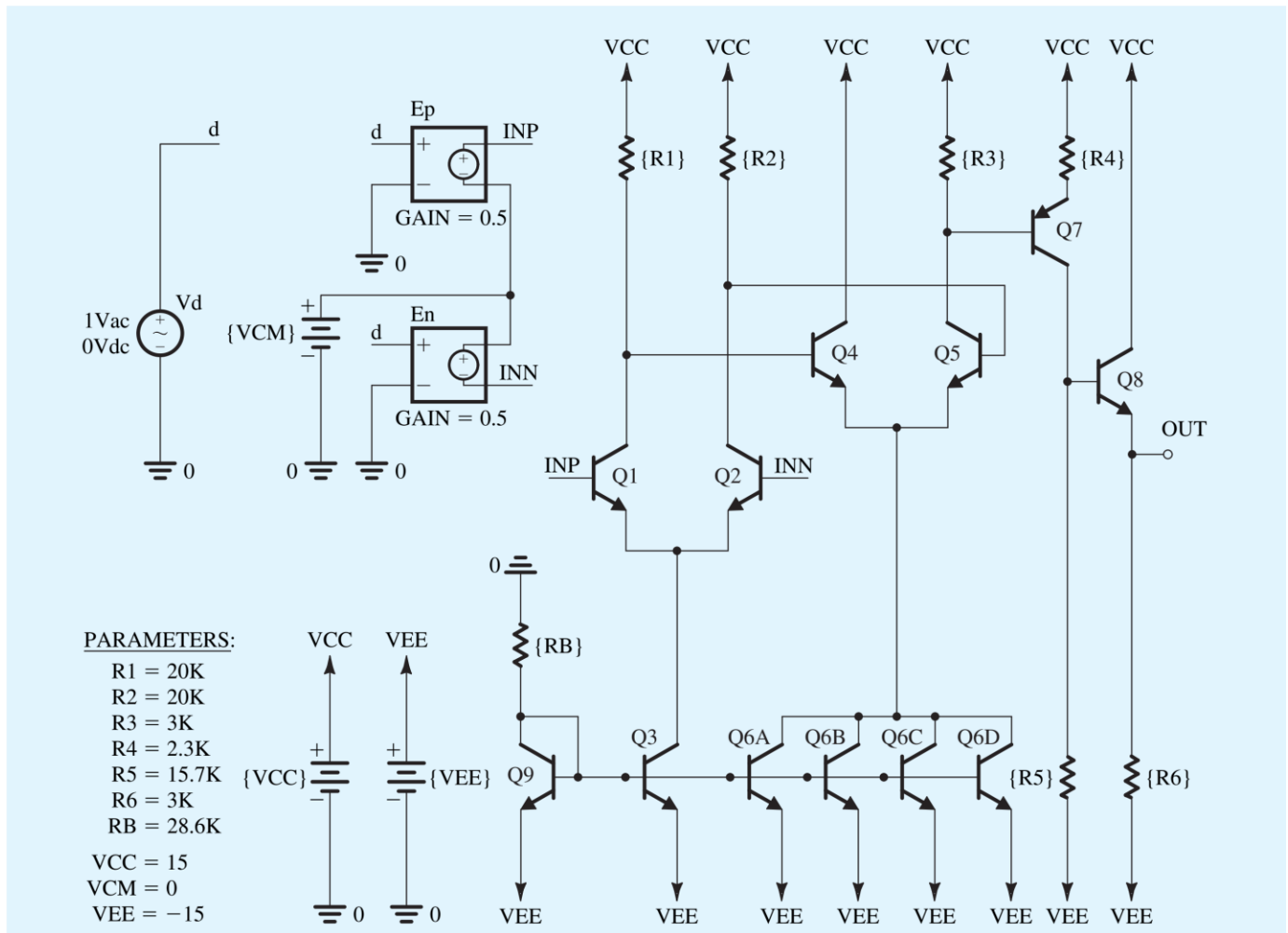


Figure 1 Schematic capture of the op-amp circuit

In this example, we will use parts Q2N3904 and Q2N3906 (from Fairchild Semiconductor) for the npn and pnp BJTs.

Each student should supply a pdf report that has results and an OrCAD project files in .zip format.

- construct the circuit shown in Figure-1.

In OrCAD, the common-mode input voltage V_{CM} of the op-amp circuit is set to 0 V (i.e., to the average of the dc power-supply voltages V_{CC} and V_{EE}) to maximize the available input signal swing. A **bias-point** simulation is performed to determine the dc operating point.

- **Construct a table that shows the collector current for each transistor.**

To compute the large-signal differential transfer characteristic of the op-amp circuit, we perform a **dc-analysis simulation** in PSpice with the differential voltage input V_d swept over the range $-V_{EE}$ to $+V_{CC}$, and we plot the corresponding output voltage V_{OUT} .

- **Plot the resulting dc transfer characteristic.**


Repeat **dc analysis** is with V_d swept over the range -5mV to $+5\text{mV}$ at increments of $10\text{ }\mu\text{V}$.

- **Plot the resulting differential dc transfer characteristic. What is the gain of op-amp?**

To compute the **frequency response** of the op-amp circuit and to measure its differential gain A_d and its 3-dB frequency f_H in OrCAD, we set the differential input voltage V_d to be a 1-V ac signal (with 0-V dc level), perform an **ac-analysis simulation**.

- **Plot the output voltage magnitude V_{OUT} versus frequency.**

Notes:

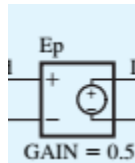

This voltage controlled voltage source that can be found in OrCAD under **ANALOG lib** with name **E**.